


#### **BUZZER**

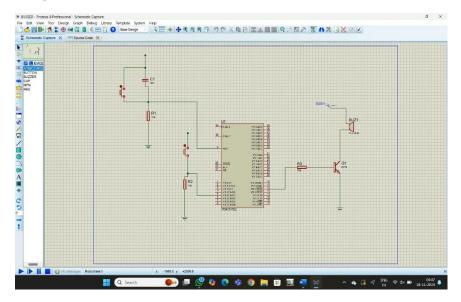


### Square wave

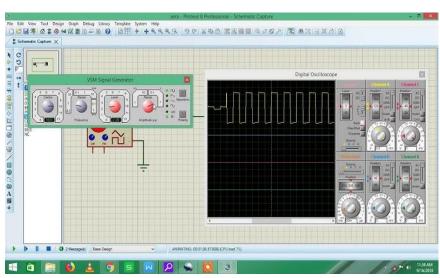


# Chaser

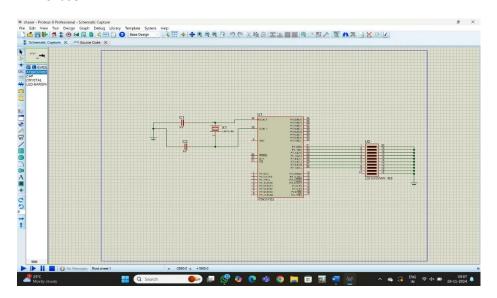


# Blinking led

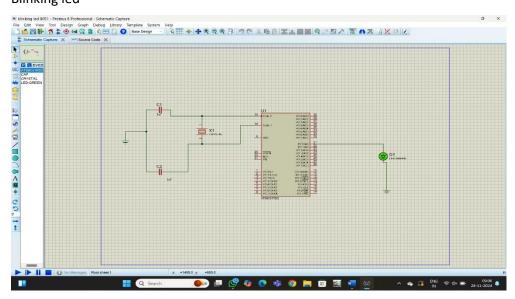


### Led bulb

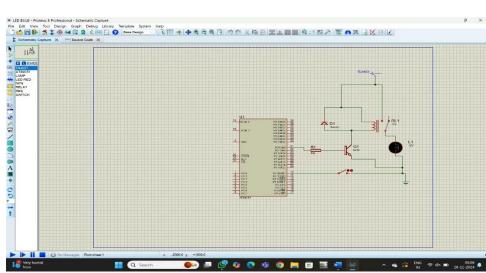


# Dc motor

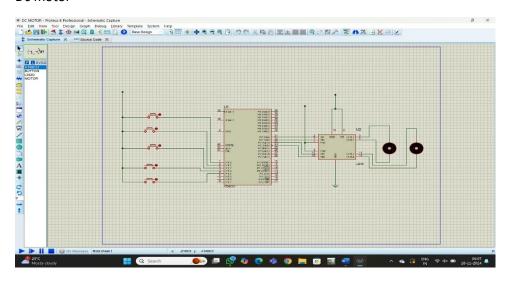


#### Clockwise

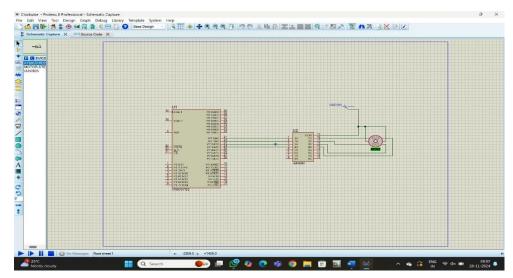


# led switching

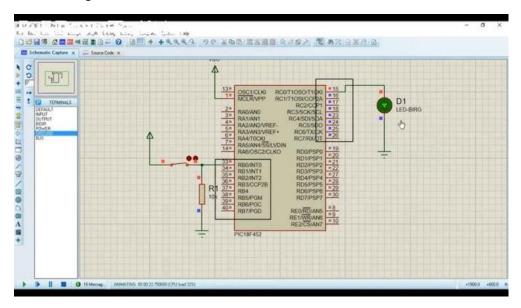


### Segment display

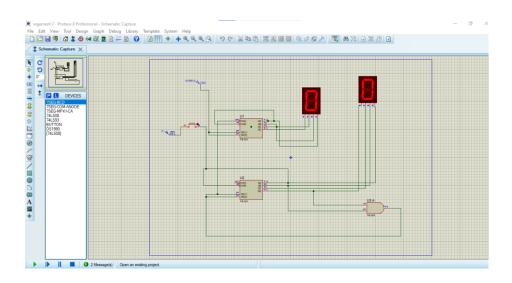

#### Fade in fade out

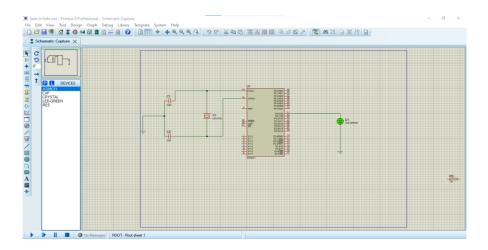

#### anticlock wise

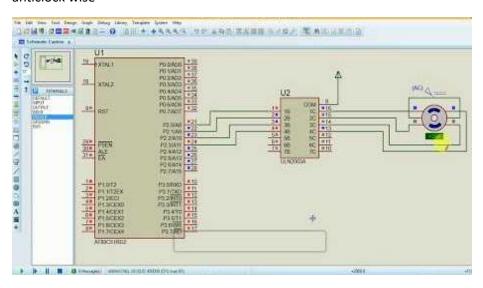

### Toggle

